1) The value of V_o is:

a) 7.4 V b) 5714 mV

c) 500 mV d) -6400 mV

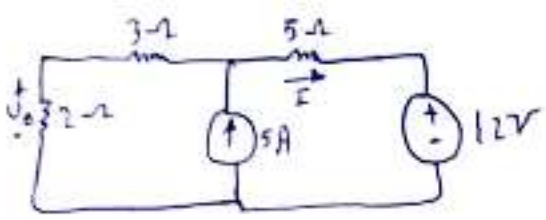


Fig. 1

2) The value of the current (i) in 5Ω is:

a) -0.75A b) 1.4A

c) 1.3A d) 0.2A

3) The power absorbed by 3Ω resister is:

a) 5.23 W b) 6.46 W

c) 10.46 W d) 41.07 W

4) The Power absorbed by 12V voltage source is:

a) 31.2 W b) 44.8 W

c) -15.6 W d) -44.8 W

Team ZerOne
Computer & Networks Engineers

Prob. 2: For question 5,6 consider the current through a 1 mH inductor i. $i(t) = 60\cos 100t$ mA.

5) The terminal voltage across the inductor is:

a) $-6\sin 100t$ mV b) $-6\cos 100t$ mV

c) -9V d) 6 mV

6) The Energy stored in the inductor is:

a) $18\sin^2(100)$ μJ b) $1.8\cos^2(100t)$ μJ

c) 180 μJ d) 18 mJ

CamScanner

Prob 3: for question 7, 8, 9, 10 consider the circuit shown in Figure 2. The switch has been closed for a long time. At $t=0$, the switch is opene

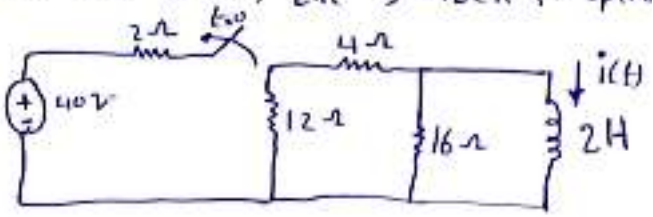


Fig.2

7) The initial current $i(t=0+)$ is:

a) 24 A b) 60 A

c) 36 A d) 6 A

8) The time constant of the circuit is:

a) 120 s b) 250 ms

c) 60 s d) 500 ms

9) The current in the inductor at $t=500$ ms is:

a) 128.8 mA b) 0.812 A

c) 606.5 mA d) 2.8 A

Team ZerOne Computer & Networks Engineers

10) The final value of the voltage $v(t=\infty)$ across the inductor is:

a) 0 V b) 36 V

c) 24 V d) 12 V

CamScanner

prob. 4: Consider the Circuit ... Figure 3. Use the Thevenin's Theorem with respect to terminals (a-b)

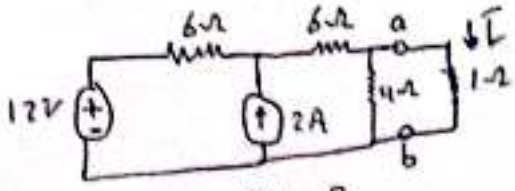


Fig 3

a. The Thevenin voltage is ——

b. The Thevenin resistance is ——

c. The current I is ——

d. what is the value of the load resistance that should be connected to the ab terminal to achieve maximum power transfer? ——

prob. 5: Consider the circuit shown in figure 4. And answer

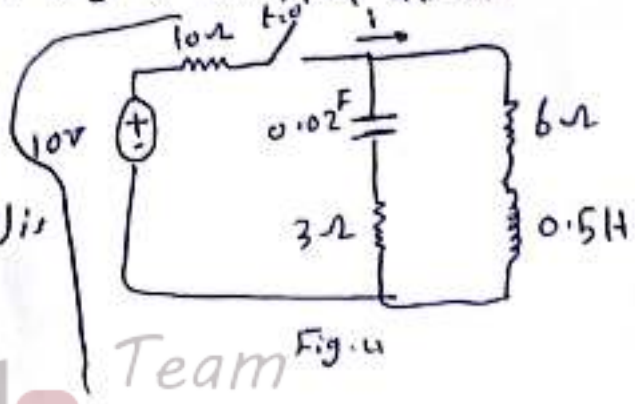


Fig. 4

a- The value of α (α (damping factor) is:

b- The value of ω_o (resonant frequency) is

c- The value of S_1 is ——


d- The value of S_2 is ——

e- The natural response i(t) for $t>0$ in general form is ——

f- The initial inductor current i(0) is ——

g- The initial capacitor voltage v(0) is ——

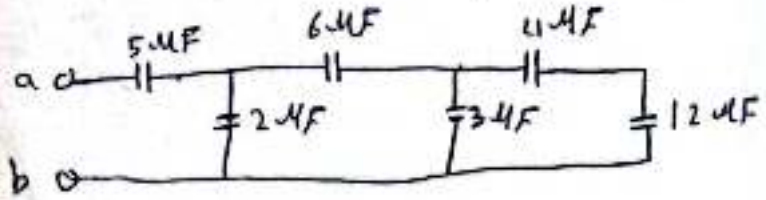prob 6: a) Refer to figure 5; the value of the equivalent capacitance is: ——



Team Zerone Computer & Networks Engineers

CamScanner

b) Refer to figure 6; the value of the equivalent resistance is

_____

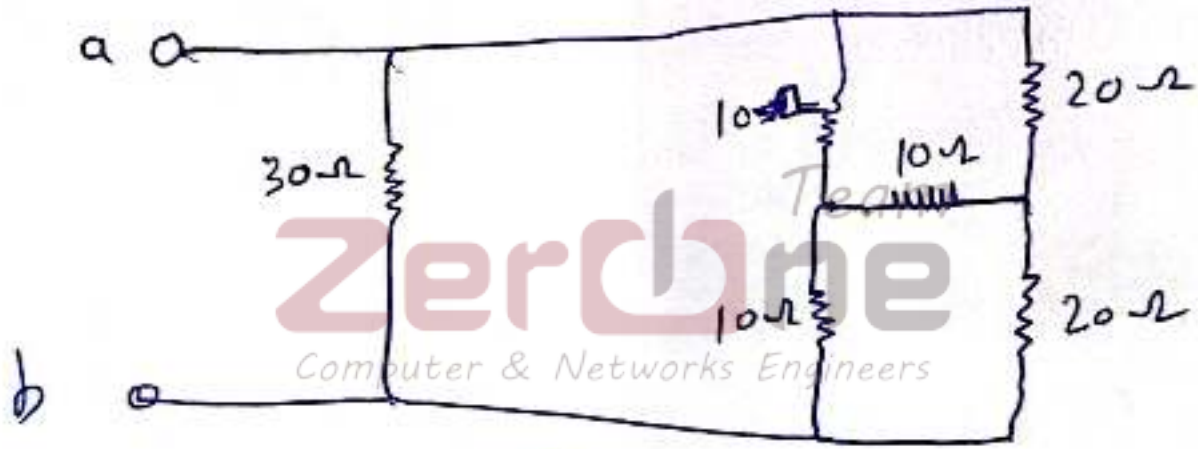


Fig. 6

ZerOne Team
Computer & Networks Engineers

CamScanner