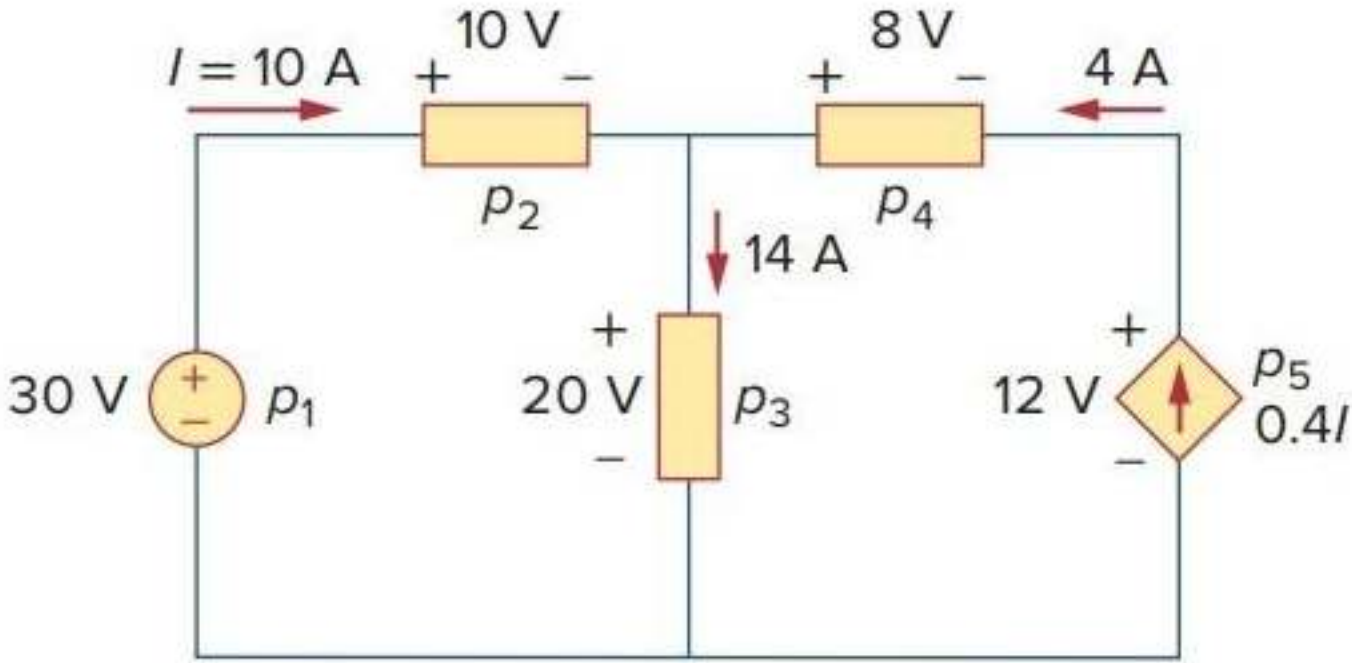Find the power absorbed by each of the elements